

Time Allotted : 3 Hours

Full Marks :70

The Figures in the margin indicate full marks.


Candidate are required to give their answers in their own words as far as practicable

Group-A (Very Short Answer Type Question)


1. Answer any ten of the following :

[1 x 10 = 10]

 
- (I) In the astable amplifier, up to what voltage the capacitor charges ?
- (II) The state 1110 is a valid state in 8-4-2-1 Binary Coded Decimal counter . State True / False.
- (III) A 4 bit mod 16 ripple counter uses JK flip-flop. If the propagation delay of each flip flop is 100 ns, what will be the maximum clock frequency (in MHz) that can be used in the counter ?
- (IV) In Asynchronous circuit Race condition always arises. State True / False.
- (V) What is the minimum number of NAND gates required to design a Full adder circuit ?
- (VI) Which type of ADC (analog-to-digital converter) is slowest of all ?
- (VII) Which A/D converters are used for High speed operation ?
- (VIII) The input of a Schmitt Trigger is sawtooth wave , what will be shape of the output?
- (IX) The output Y of the logic circuit given below is _____



 - (X) Five JK flip - flops are cascaded to form circuit shown in figure. Clock pulses at a frequency of 1 MHz are applied as shown. What will be the frequency (in kHz) of the waveform at Q₃ ?



- (XI) If $(212)_X - (23)_{10}$, where X is the base of the number system , find X
- (XII) A mod-n counter using a synchronous binary up-counter with synchronous clear input is shown in the figure. What will be the value of n ?

  

Group-B (Short Answer Type Question)

Answer any three of the following


[5 x 3 = 15]

2. Perform Conversion of D flip Flop to J-K Flip Flop [5]
3. Perform conversion of S-R Flip flop to J-K Flip Flop [5]
4. Design a 5 to 32 decoder using 3 to 8 decoder and 2 to 4 decoder. [5]

5. Figure shows a 4 to 1 MUX to be used to implement the sum S of a 1-bit full adder with input bits P and Q and the carry input C_{in} . Find the combinations of inputs to I_0, I_1, I_2 and I_3 of the MUX which will realize the sum S [5]



 6. Find the oscillation frequency f of the phase shift oscillator when $R = 10K\Omega$ and $C = 6.5nf$ [5]




Group-C (Long Answer Type Question)


Answer any three of the following

[15 x 3 = 45]

 
7. (a) In the given MUX the output is $F = A \text{ XOR } B$. What will be the inputs I_0, I_1, I_2, I_3 ? [5]



 - (b) Check the following digital circuit. What will be the equivalent logic gate of the whole circuit ? [5]




 - (c) What will be minimised output F of the circuit [5]




8. (a) Define Voltage , Current and Power amplifier [3]
 (b) Write the different classes of Power amplifier [3]
 (c) Draw the circuit diagram of a class B push pull transistor amplifier Explain the operation [5]
 (d) Derive the maximum efficiency of a class B amplifier [4]

 
9. (a) To realize the given truth table from the circuit shown in the figure, find the input to J in terms of A and B. [7]



 - (b) What is the equivalent flip-flop of the digital circuit given below ; explain with reason. [4]



 
- (c) The clock frequency applied to the digital circuit shown in the figure below is 1KHz. If the initial state of the output of the flip-flop is 0, what will be the frequency of the output waveform Q in KHz ? [4]



10. (a) Find the simplified form of the Boolean expression Y , where [8]

$$Y = (A'BC + D)(A'D + B'C')$$

 - (b) The output F of decoder can be realised with best logic gates. Find out the Boolean expression. [7]



11. (a) Draw the circuit diagram of a Astable Multivibrator using IC 555 timer [6]

- (b) Derive the expression duty cycle and frequency of oscillation [6]

- (c) Explain why this is called Free running oscillator. [3]